

Specification and Simulation of Combinational Designs using VHDL

With thanks to Sudhakar Yalamanchili

Overview

1. Introduction to VHDL

- Use in describing systems

2. Describing & modelling systems

- Interface & behaviour
- Signals, events, timing, concurrency
- Use of discrete event simulation

3. Basic language constructs


- Std_logic resolved type
- Signal assignments
- Delays
- Modelling complex behaviour
- Modelling structure

4. Use of VHDL to model and simulate sequential logic designs

1. Introduction to VHDL


- **Use in describing systems**

Describing Digital Systems

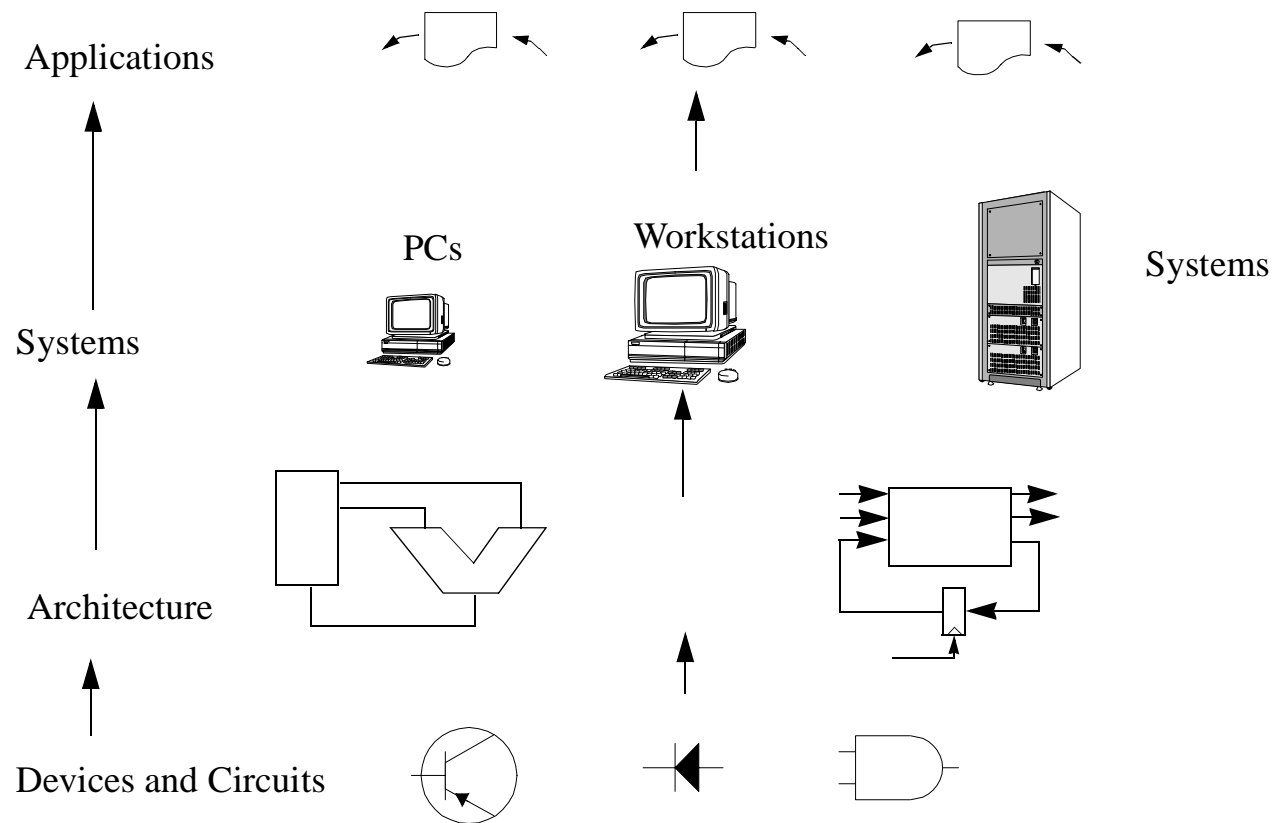

- Systems may be described at multiple levels of abstraction


The Digital System Design Process

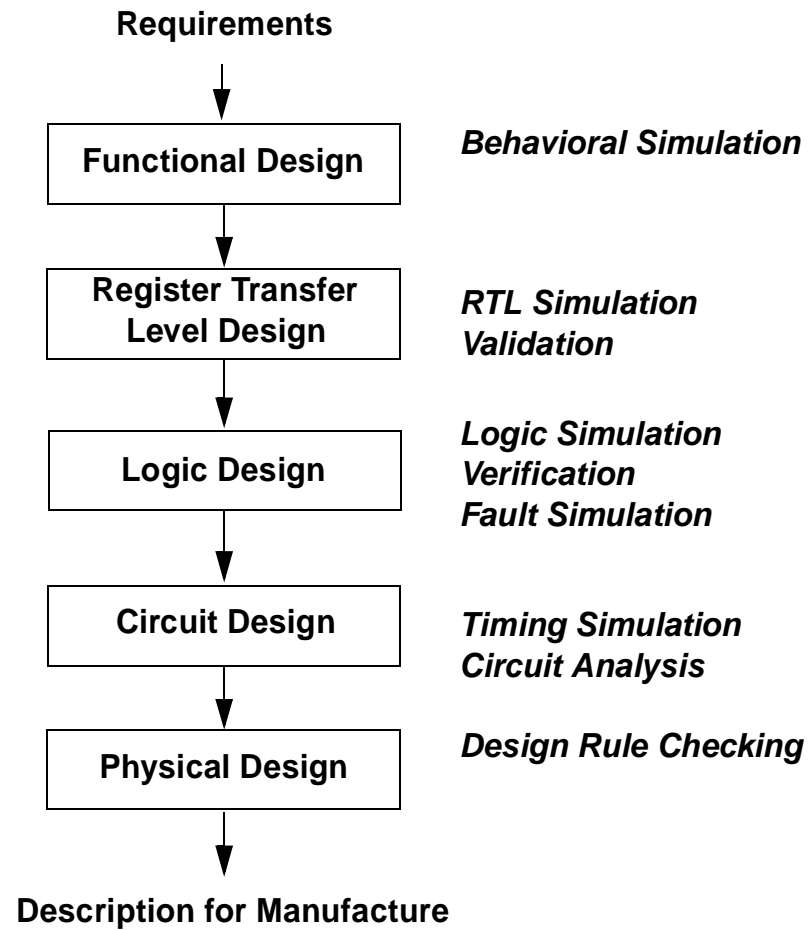

Why Do We Describe Systems?

- Design Specification
 - unambiguous definition of components and interfaces in a large design
- Design Simulation
 - verify system/subsystem/chip performance prior to design implementation
- Design Synthesis
 - automated generation of a hardware design

Hardware Description Languages

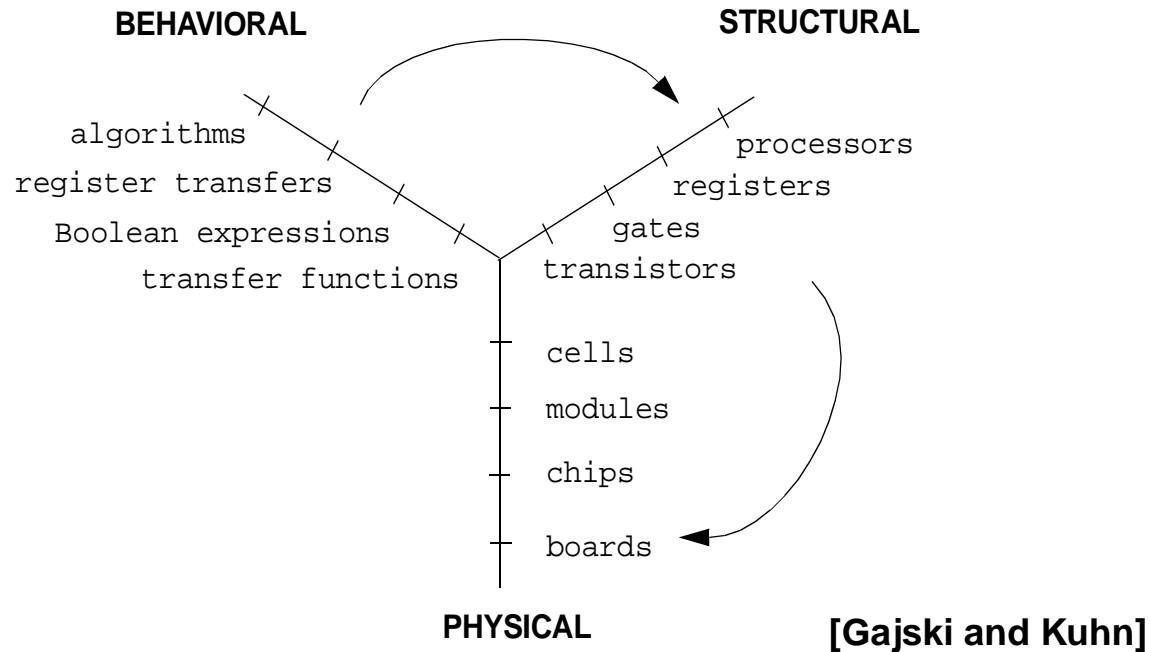

- Design is structured around a hierarchy of representations
- HDLs can describe distinct aspects of a design at multiple levels of abstraction

The VHDL Language

V *Very High Speed Integrated Circuit*

H *Hardware*

D *Description*

L *Language*

- Interoperability between design tools: standardized portable model of electronic systems
- Technology independent description
- Reuse of components described in VHDL


History of VHDL

- Designed by IBM, Texas Instruments, and Intermetrics as part of the DoD funded VHSIC program
- Standardized by the IEEE in 1987: IEEE 1076-1987
- Enhanced version of the language defined in 1993: IEEE 1076-1993
- Additional standardized packages provide definitions of data types and expressions of timing data
 - IEEE 1164 (data types)
 - IEEE 1076.3 (numeric)
 - IEEE 1076.4 (timing)

2. Describing & modelling systems


- **Interface & behaviour**
- **Signals, events, timing, concurrency**
- **Use of discrete event simulation**

Describing Systems

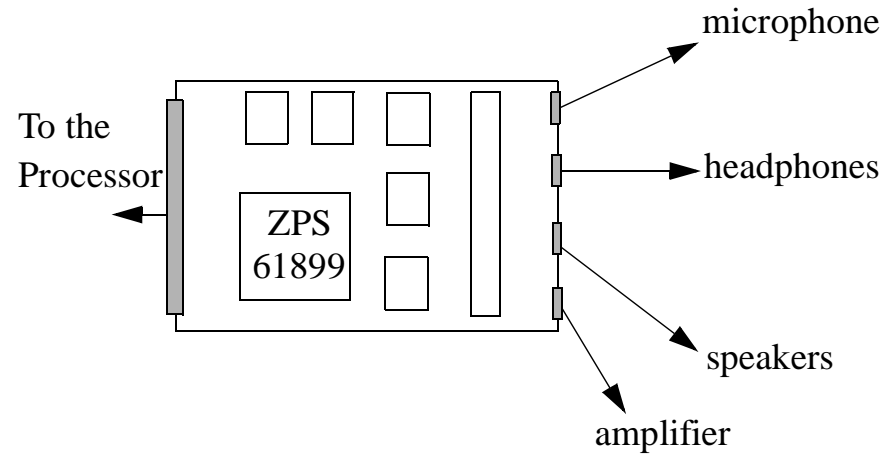


- System: “An assemblage of objects united by some form or regular interaction or dependence”
- What aspects of a digital system do we want to describe?
 - interface
 - behavior: functional and structural

Basic Language Concepts

 

- What aspects of a digital system do we want to describe?
 - interface: how do we connect to it
 - behavior: what does it do?

 
Describing the Interface: The Entity Construct



```
entity half_adder is  
port ( a, b : in bit;  
        sum, carry : out bit);  
end half_adder ;
```

- The interface is a collection of *ports*
 - ports are a new programming object: *signal*
 - ports have a type, e.g., **bit**
 - ports have a mode: in, out, inout (bidirectional)


Example Entity Descriptions

 

```

entity ALU32 is
port( A, B: in bit_vector (31 downto 0);
      C: out bit_vector (31 downto 0);
      Op: in bit_vector (5 downto 0);
      N, Z: out bit);
end ALU32;

```

 


```

entity D_ff is
port( D, Q, Clk, R, S: in bit;
      Q, Qbar: out bit);
end D_ff;

```

 Describing Behavior: The Architecture Construct




```
entity half_adder is  
port (a, b : in bit;  
       sum, carry : out bit);  
end half_adder;
```

```
architecture behavioral of half_adder  
is  
begin  
  sum <= (a xor b) after 5 ns;  
  carry <= (a and b) after 5 ns;  
end behavior;
```



- Description of events on output signals in terms of events on input signals: the *signal assignment statement*
- Specification of propagation delays
- Type **bit** is not powerful enough for realistic simulation: use the IEEE 1164 value system

Behavioral Attributes of Digital Systems

 


- Digital systems are about *signals* and their *values*
- *Events, propagation delays, concurrency*
- Time ordered sequence of events produces a *waveform*

Behavioral Attributes of Digital Systems

 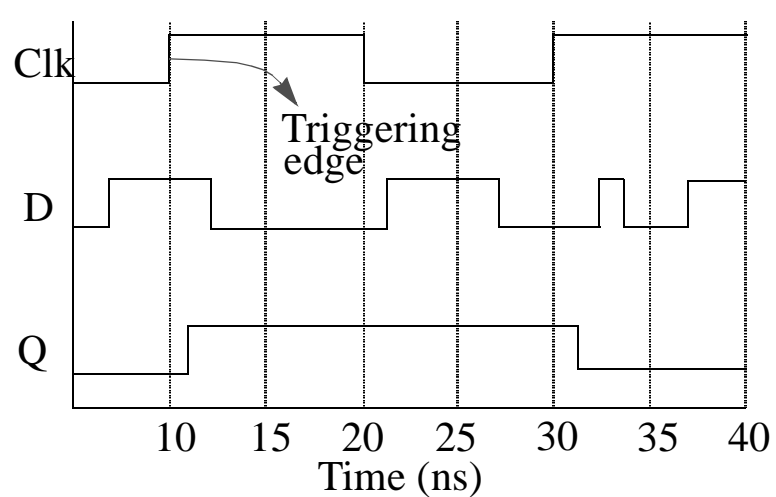




- *Timing*: computation of events takes place at specific points in time
- Timing is an attribute of both synchronous and asynchronous systems

Simulation of Digital Systems

 


- Digital systems propagate events
- Discrete event simulations manage the generation and recording of events

Simulation Modeling

   


*HDL
Description*

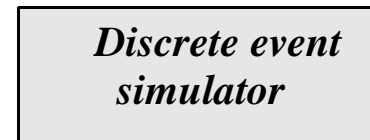

Altera, Viewlogic, Xilinx

- VHDL programs describe the generation of events in digital systems
- Discrete event simulator manages event ordering and progression of time

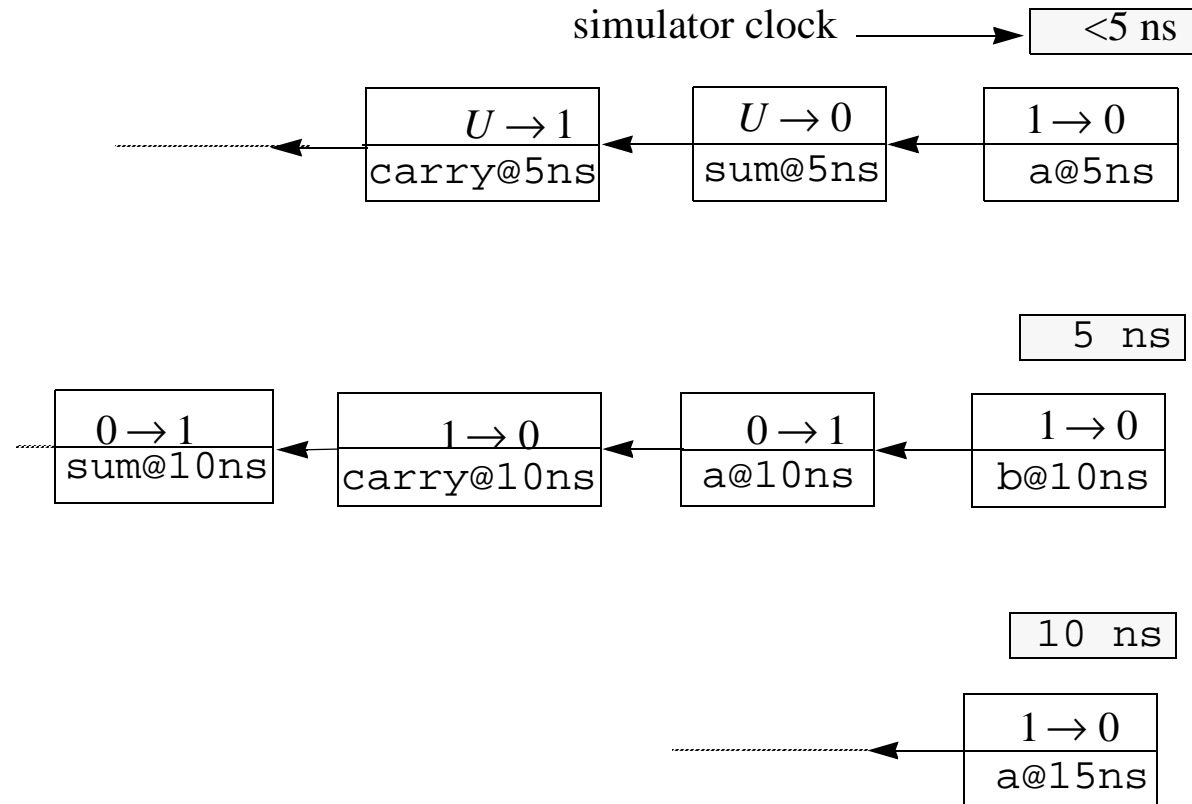Discrete Event Simulation: Half Adder Model.



- Management of simulation time: ordering of events
- Two step model of the progression of time

Discrete Event Simulation Algorithm

repeat until event_list empty or preset simulation time expired:

- 1. Advance simulation time to that of the next event (earliest timestamp in the event list) and process all events (update all signals receiving values) at this time**
- 2. Evaluate all components affected by signal updates and schedule any future events generated by inserting them into the event list**


Modeling Digital Systems

- VHDL programs describe behavioral attributes of digital systems
 - events, propagation delays, concurrency
 - waveforms and timing
 - signal values
- Discrete event simulators mimic the operation of the system being described
 - two step model of time
 - assign values scheduled for signals at the current time
 - process affected components and schedule future signal values
 - ensures events are generated and processed in the correct order
 - a correct simulation generates *only and all* those events that would have been generated in the physical system

 3. Basic language constructs

- **Std_logic resolved type**
- **Signal assignments**
- **Delays**
- **Modelling complex behaviour**
- **Modelling structure**

Describing Behavior: The Architecture Construct




```
entity half_adder is  
port (a, b : in bit;  
       sum, carry : out bit);  
end half_adder;
```

```
architecture behavioral of half_adder  
is  
begin  
  sum <= (a xor b) after 5 ns;  
  carry <= (a and b) after 5 ns;  
end behavior;
```

- Description of events on output signals in terms of events on input signals: the *signal assignment statement*
- Specification of propagation delays
- Type **bit** is not powerful enough for realistic simulation: use the IEEE 1164 value system

Behavioral Attributes of Digital Systems

 - We associate logical values with the state of a signal




- Signal Values: IEEE 1164 Value System

Value	Interpretation
U	Uninitialized
X	Forcing Unknown
0	Forcing 0
1	Forcing 1
Z	High Impedance
W	Weak Unknown
L	Weak 0
H	Weak 1
-	Don't Care


Implementation of Signals

 - The structure of a signal assignment statement
 - $signal \leq (value\ expression\ after\ time\ expression)$
 - RHS is referred to as a *waveform element*
- Every signal has associated with it a *driver*



- holds the current and future values of the signal - a *projected waveform*
- signal assignment statements modify the driver of a signal
- value of a signal is the value at the head of the driver
- note the hardware analogy

Shared Signals

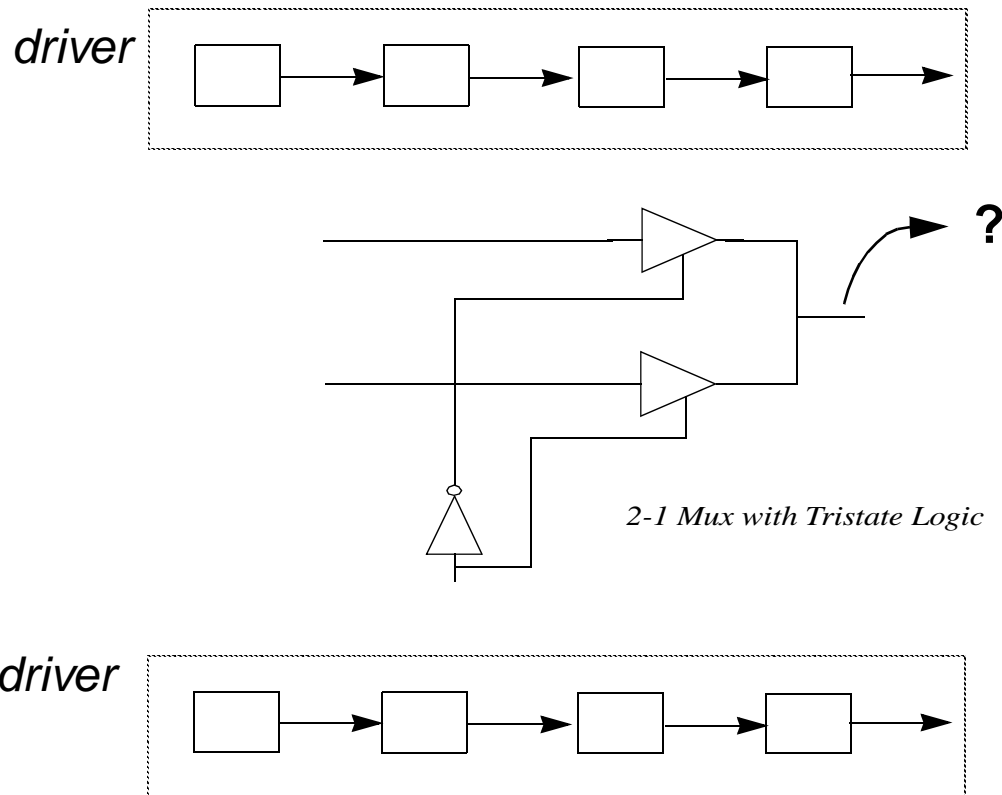

- How do we model the state of a wire?
- Rules for determining the signal value is captured in the resolution function


Resolution Function: std_logic & resolved()

- resolving values for std_logic types


	U	X	0	1	Z	W	L	H	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	X	0	0	0	0	X
1	U	X	X	1	1	1	1	1	X
Z	U	X	0	1	Z	W	L	H	X
W	U	X	0	1	W	W	W	W	X
L	U	X	0	1	L	W	L	W	X
H	U	X	0	1	H	W	W	H	X
-	U	X	X	X	X	X	X	X	X

- Pairwise resolution of signal values from multiple drivers
- Resolution operation must be associative

Example Entity Descriptions: IEEE 1164

 

 
```
entity ALU32 is
port( A,B: in std_logic_vector (31 downto 0);
      C: out std_logic_vector (31 downto 0);
      Op: in std_logic_vector (5 downto 0);
      N,Z: out std_logic);
end ALU32;
```



```
entity D_ff is
port( D,Q,Clk,R,S: in std_ulogic;
      Q,Qbar: out std_ulogic);
end D_ff;
```

 Describing Behavior: The Architecture Construct




```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity half_adder is  
port ( a, b : in std_logic;  
        sum, carry : out std_logic);  
end half_adder;
```

```
architecture behavioral of half_adder  
is  
begin  
sum <= (a xor b) after 5 ns;  
carry <= (a and b) after 5 ns;  
end behavioral;
```

- Use of the IEEE 1164 value system simply requires inclusion of the library and package declarations statements

Design Units

 


- An entity may have multiple architectures
- Separation of interface from implementation

Simple Signal Assignment

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity full_adder is  
    port (in1, in2, c_in: in std_logic;  
          sum, c_out: out std_logic);  
end full_adder;
```

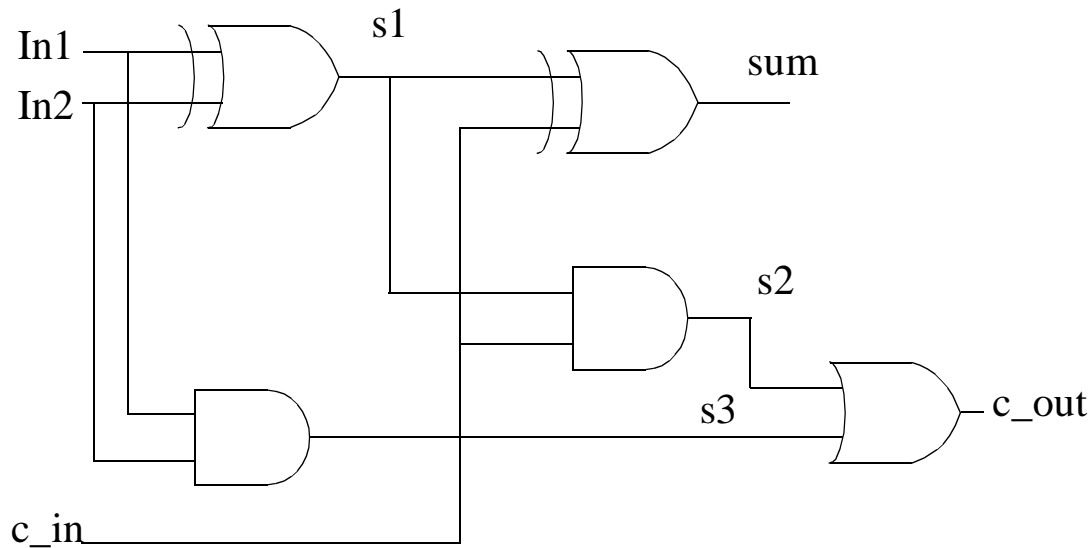
```
architecture dataflow of full_adder is  
    signal s1, s2, s3 : std_logic;  
    constant gate_delay: Time:= 5 ns;  
begin  
    L1: s1 <= (In1 xor In2) after gate_delay;  
    L2: s2 <= (c_in and s1) after gate_delay;  
    L3: s3 <= (In1 and In2) after gate_delay;  
    L4: sum <= (s1 xor c_in) after gate_delay;  
    L5: c_out <= (s2 or s3) after gate_delay;  
end dataflow;
```



Simple Signal Assignment Statement

- The *constant* programming object
 - values cannot be changed
- Use of signals in the architecture
 - internal signals used to connect components
- A statement is executed when a signal in the RHS has value assigned to it
 - 1-1 correspondence between signal assignment statements and signals in the circuit
 - order of statement execution follows propagation of events in the circuit
 - textual order *does not* imply execution order
 - trace the statement execution order when In1 changes value

Understanding Delays

 



- Inertial delay model
- Transport delay model
- Delta delay model

Understanding Delays

- Inertial delay
 - default delay model
 - suitable for modeling delays through devices such as gates
- Transport Delay
 - to model delays through devices with very small inertia, e.g, wires
 - all input events are propagated to output signals
- Delta delay
 - what about models where no propagation delays are specified?
 - infinitesimally small delay is automatically inserted by the simulator to preserve correct ordering of events

Transport Delays: Example

  
```
architecture transport_delay of
half_adder is
signal s1, s2: std_logic:= '0';
begin
s1 <= (a xor b) after 2 ns;
s2 <= (a and b) after 2 ns;
sum <= transport s1 after 4 ns;
carry <= transport s2 after 4 ns;
end transport_delay;
```




Delta Delays: Example

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity combinational is  
  port (In1, In2: in std_logic;  
        z : out std_logic);  
end combinational;
```
 
```
architecture behavior of  
combinational is  
  signal s1, s2, s3, s4: std_logic:=  
begin  
  s1 <= not In1;  
  s2 <= not In2;  
  s3 <= not (s1 and In2);  
  s4 <= not (s2 and In1);  
  z <= not (s3 and s4);  
end behavior;
```




Delta Delays: Example

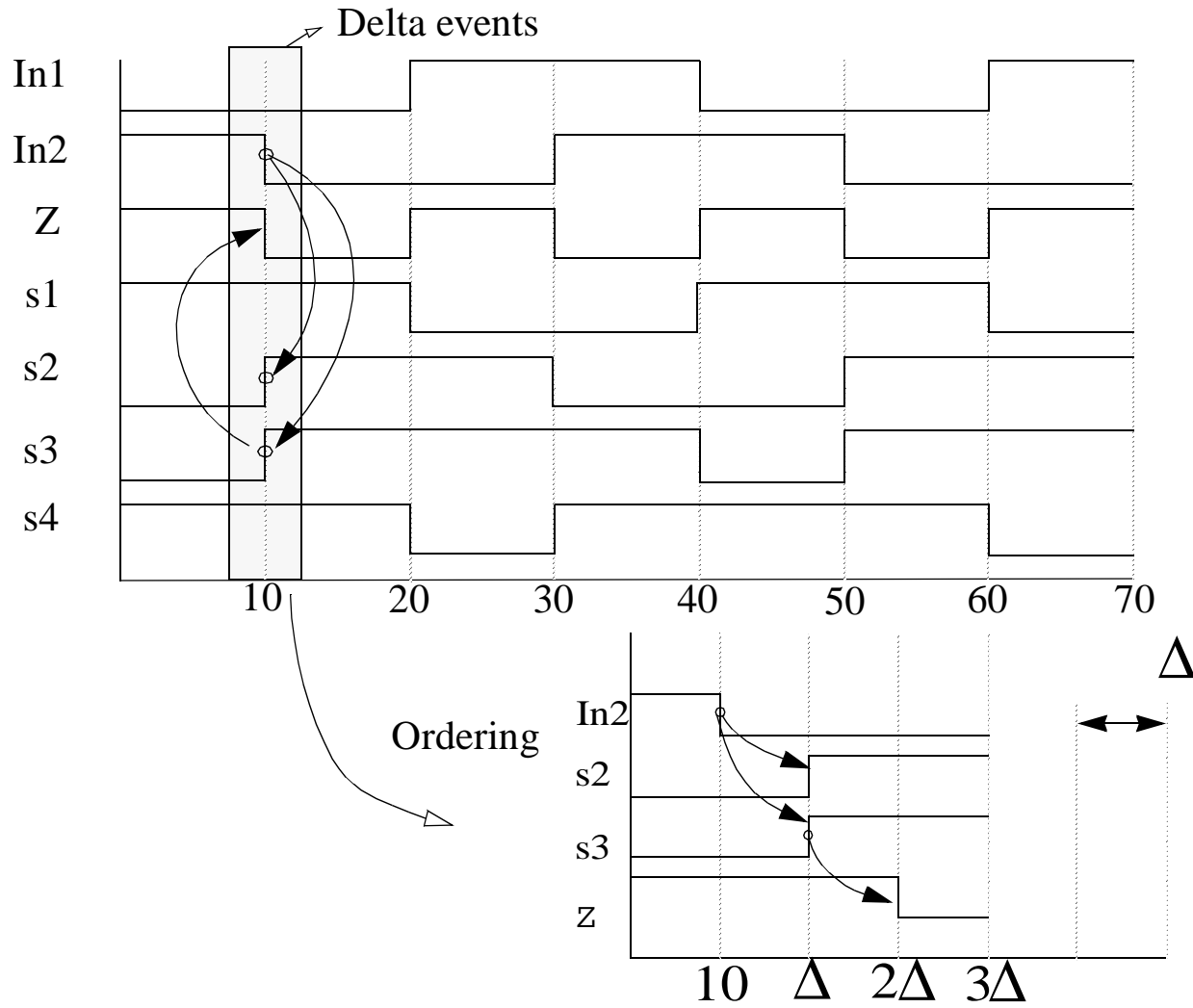

Conditional Signal Assignment

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port (  In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
       Sel: in std_logic_vector(1 downto 0);
       Z : out std_logic_vector (7 downto 0));
end mux4;

 architecture behavioral of mux4 is
begin
Z <= In0 after 5 ns when Sel = "00" else
     In1 after 5 ns when Sel = "01" else
     In2 after 5 ns when Sel = "10" else
     In3 after 5 ns when Sel = "11" else
     "00000000" after 5 ns;
end behavioral;
```



Evaluation order
is important!

- First true conditional determines the output value

Selected Signal Assignment Statement

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port (   In0, In1, In2, In3  : in std_logic_vector (7 downto 0);
        Sel: in std_logic_vector(1 downto 0);
        Z  : out std_logic_vector (7 downto 0));
end mux4;
```


```
architecture behavioral-2 of mux4 is
```

```
begin
```

```
with Sel select
```

```
Z <= (In0 after 5 ns) when "00",
      (In1 after 5 ns) when "01",
      (In2 after 5 ns) when "10",
      (In3 after 5 ns) when "11"
      (In3 after 5 ns) when others;
```


```
end behavioral;
```

 

All options must be covered and only one must be true!

- The “when others” clause can be used to ensure that all options are covered

Modeling Complex Behavior

 

Memory Module

add R1, R2, R3

sub R3, R4, R5

move R7, R3

•

•

•

Instruction Set Simulation

- Concurrent signal assignment statements can easily capture the gate level behavior of digital systems
- Higher level digital components have more complex behaviors
 - input/output behavior not easily captured by concurrent signal assignment statements
 - models utilize state information
 - incorporate data structures
- We need more powerful constructs

The Process Statement

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity mux4 is  
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);  
       Sel: in std_logic_vector(1 downto 0);  
       Z : out std_logic_vector (7 downto 0));  
end mux4;
```

```
architecture behavioral-3 of mux4 is
```

```
begin
```

```
process (Sel, In0, In1, In2, In3)
```

Sensitivity List

```
variable Zout: std_logic;
```

```
begin
```

```
    if (Sel = "00") then Zout:= In0;
```

```
    elsif (Sel = "01") then Zout:= In1;
```

```
    elsif (Sel = "10") then Zout:= In2;
```

```
    else Zout:= In3;
```

```
    end if;
```

```
    Z <= Zout;
```

Variable Assignment


```
end process;
```

```
end behavioral;
```

The Process Construct

- Statements in a process are executed sequentially
- A process body is structured much like conventional C or Pascal programs
 - declaration and use of variables
 - *if-then, if-then-else, case, loop and while* constructs
 - process can contain signal assignment statements
- A process executes concurrently with other concurrent signal assignment statements
- A process takes 0 simulation time to execute and may schedule events in the future: we can think of a process as a complex signal assignment statement!

Concurrent Processes: Full Adder

 

- Each of the components of the full adder can be modeled using a process
- Processes execute concurrently
- Processes communicate via signals

Concurrent Processes: Full Adder

```
library IEEE;
use IEEE.std_logic_1164.all;

entity full_adder is
port (In1, c_in, In2 : in std_logic;
      sum, c_out : out std_logic);
end full_adder;

architecture behavioral of
full_adder is
signal s1, s2, s3: std_logic;
constant delay :Time:= 5 ns;
begin
HA1: process (In1, In2)
begin
s1 <= (In1 xor In2) after delay;
s3 <= (In1 and In2) after delay;
end process HA1;

HA2: process(s1,c_in)
begin
sum <= (s1 xor c_in) after
delay;
s2 <= (s1 and c_in) after delay;
end process HA2;

OR1: process (s2, s3) -- process
describing the two-input OR gate
begin
c_out <= (s2 or s3) after delay;
end process OR1;
end behavioral;
```

Concurrent Processes: Half Adder

```
library IEEE;
use IEEE.std_logic_1164.all;

entity half_adder is
port (a, b: in std_logic;
sum, carry: out std_logic);
end half_adder;

architecture behavior of
half_adder is
begin
sum_proc: process(a,b)
begin
if (a = b) then
sum <= '0' after 5 ns;
else
sum <= (a or b) after 5 ns;
end if;
end process;

carry_proc: process (a,b)
begin
case a is
when '0' =>
carry <= a after 5 ns;
when '1' =>
carry <= b after 5 ns;
when others =>
carry <= 'X' after 5 ns;
end case;
end process carry_proc;
end behavior;
```

The Wait Statement

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity dff is  
port (D, Clk : in std_logic;  
      Q, Qbar : out std_logic);  
end dff;
```

```
architecture behavioral of dff is
```

```
begin
```

```
output: process
```

```
begin
```

```
wait until (Clk'event and Clk = '1'); -- wait for edge
```


```
    Q <= D after 5 ns;
```

```
    Qbar <= not D after 5 ns;
```

```
end process output;
```

```
end behavioral;
```

*signifies a value change
on signal clk*



- wait for *<time expression>*, wait on *<signal>*, wait until *<boolean expression>*


The Wait Statement: Waveform Generation

```
library IEEE;
use IEEE.std_logic_1164.all;
entity two_phase is
port(phi1, phi2, reset: out
std_logic);
end two_phase;

architecture behavioral of
two_phase is
begin
rproc: reset <= '1', '0' after 10 ns;

clock_process: process
begin
phi1 <= '1', '0' after 10 ns;
phi2 <= '0', '1' after 12 ns, '0' after
18 ns;
wait for 20 ns;
end process clock_process;
end behavioral;
```

 
*events specified
by the reset
and clock
processes*



The Wait Statement



- A process can have multiple wait statements
- A process cannot have both a wait statement and a sensitivity list (it should have one or the other)

Modeling Structure

 

- Structural models describe a digital system as an interconnection of components
- Descriptions of the components must be available as structural or behavioral models

Modeling Structure

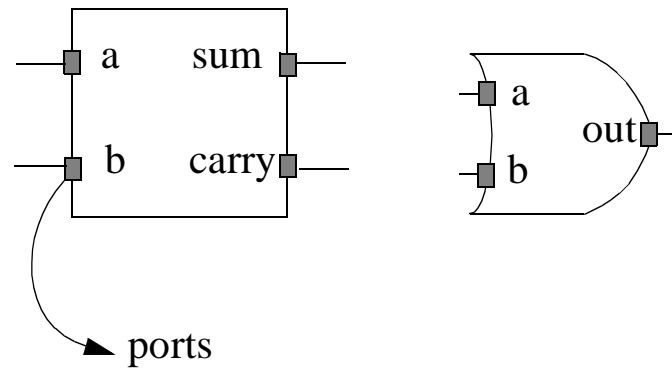 

- Define the components used in the design
- Describe the interconnection of these components

Modeling Structure

```
architecture structural of full_adder is  
component half_adder                    -- the declaration  
port (a, b: in std_logic;              -- of components you will use  
       sum, carry: out std_logic);  
end component;  
  
component or_2  
port (a, b: in std_logic;  
       c: out std_logic);  
end component;  
  
signal s1, s2, s3: std_logic;  
begin  
H1: half_adder port map (a => In1, b => In2, sum=>s1, carry=>s3);  
H2: half_adder port map (a => s1, b => c_in, sum => sum,  
                          carry => s2);  
O1: or_2 port map (a => s2, b => s3, c => c_out);  
end structural;
```

unique name of the components

component type

interconnection of the component ports

component instantiation statement

- Entity/architecture for half_adder and or_2 must exist

Hierarchy and Abstraction

architecture structural of half_adder is

component xor2

```
port (a, b : in std_logic;  
      c : out std_logic);
```

end component;

component and2

```
port (a, b : in std_logic;  
      c : out std_logic);
```

end component;

begin


```
EX1: xor2 port map (a => a, b => b, c => sum);
```

```
AND1: and2 port map (a=> a, b=> b, c=> carry);
```

end structural;

- Structural descriptions can be nested
- The half adder may itself be a structural model

Hierarchy and Abstraction

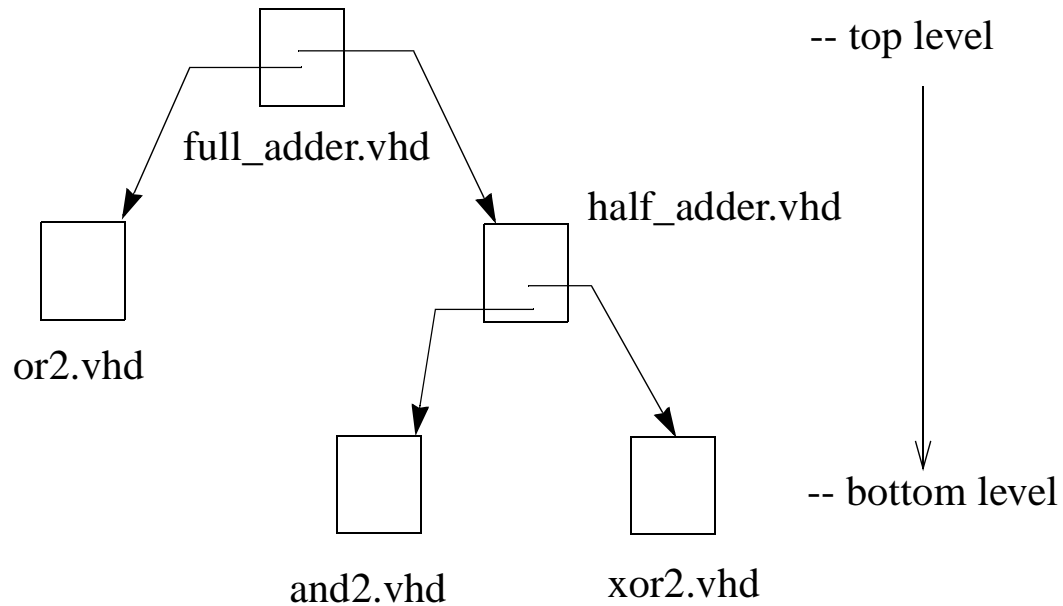

- Nested structural descriptions to produce hierarchical models
- The hierarchy is flattened prior to simulation
- Behavioral models of components at the bottom level must exist

Generics

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity xor2 is  
generic (gate_delay : Time:= 2 ns);  
port(In1, In2 : in std_logic;  
      z : out std_logic);  
end xor2;  
  
architecture behavioral of xor2 is  
begin  
z <= (In1 xor In2) after gate_delay;  
end behavioral;
```

- Enables the construction of parameterized models

Generics in Hierarchical Models


```
architecture generic_delay of half_adder is  
component xor2  
generic (gate_delay: Time);  
port (a, b : in std_logic;  
       c : out std_logic);  
end component;
```

```
component and2  
generic (gate_delay: Time);  
port (a, b : in std_logic;  
       c : out std_logic);  
end component;
```


```
begin  
EX1: xor2 generic map (gate_delay => 6 ns)  
       port map(a => a, b => b, c => sum);  
A1: and2 generic map (gate_delay => 3 ns)  
       port map(a=> a, b=> b, c=> carry);  
end generic_delay;
```

- Parameter values are passed through the hierarchy


Example: Full Adder

 

full_adder.vhd

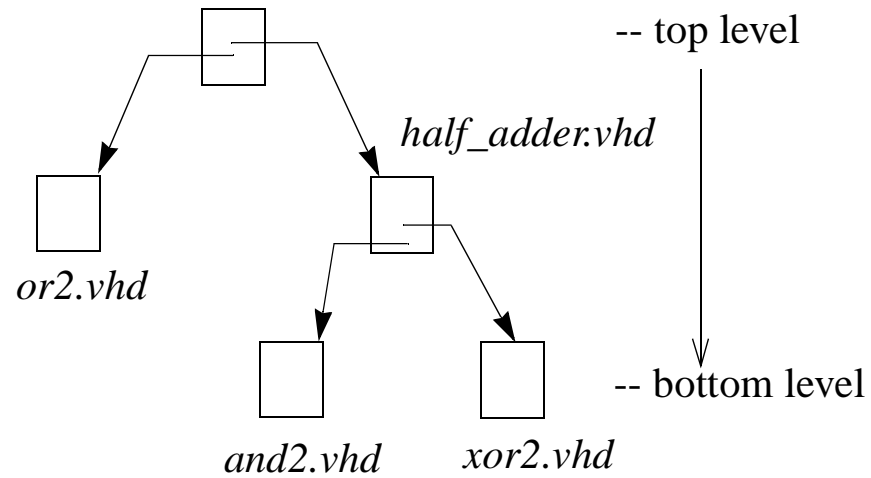

Example: Full Adder

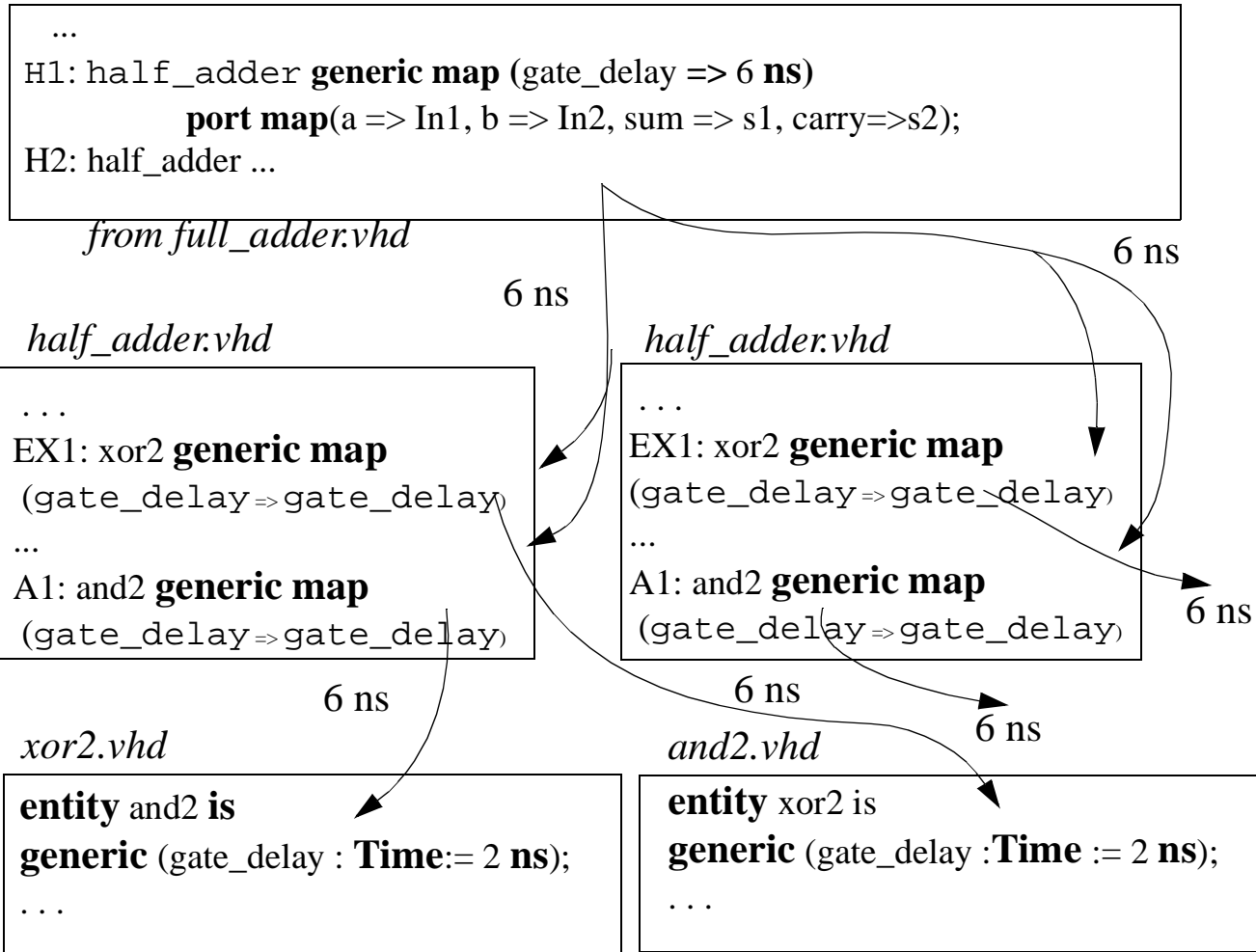

Precedence of Generic Declarations

```
architecture generic_delay2 of half_adder is
  component xor2
  generic (gate_delay: Time);
  port(a, b : in std_logic;
        c : out std_logic);
  end component;
```

```
→ component and2
  generic (gate_delay: Time:= 6 ns);
  port (a, b : in std_logic;
        c : out std_logic);
  end component;
```

takes precedence

```
begin
  EX1: xor2 generic map (gate_delay => gate_delay)
    port map(a => a, b => b, c => sum);
  → A1: and2 generic map (gate_delay => 4 ns)
    port map(a=> a, b=> b, c=> carry);
  end generic_delay2;
```

- Generic map takes precedence over the component declaration

Further reading

- **VHDL Starter's Guide, Sudhakar Yalamanchili**
- **Check the VHDL references link from the course web page**
- **Look at the on-line documentation available with ISE – there is a huge VHDL manual**
- **There are many on-line VHDL tutorials available**

Homework

1. Download and install WebPack and ModelSim as described on the VHDL references course web page,

OR

Access the ISE Project Manager from a *vmware* enabled school Linux workstation;

AND

2. Familiarize yourself with the design environment by completing the Tutorial and testing the designs we have discussed in lectures.